

GATE 2026

NIGHT WARRIORS

**3 NIGHTS ONE MISSION
TOP RANK**

**NETWORK THEORY, DIGITAL ELECTRONICS,
CONTROL SYSTEM, SIGNAL & SYSTEMS,
ANALOG ELECTRONICS**

ECE/EE

SILENCE OUTSIDE CLARITY INSIDE



Question



#Q. Find the number of combination of A, B, C for which Y will be 1.


A 4

B 5

C 6

D 7
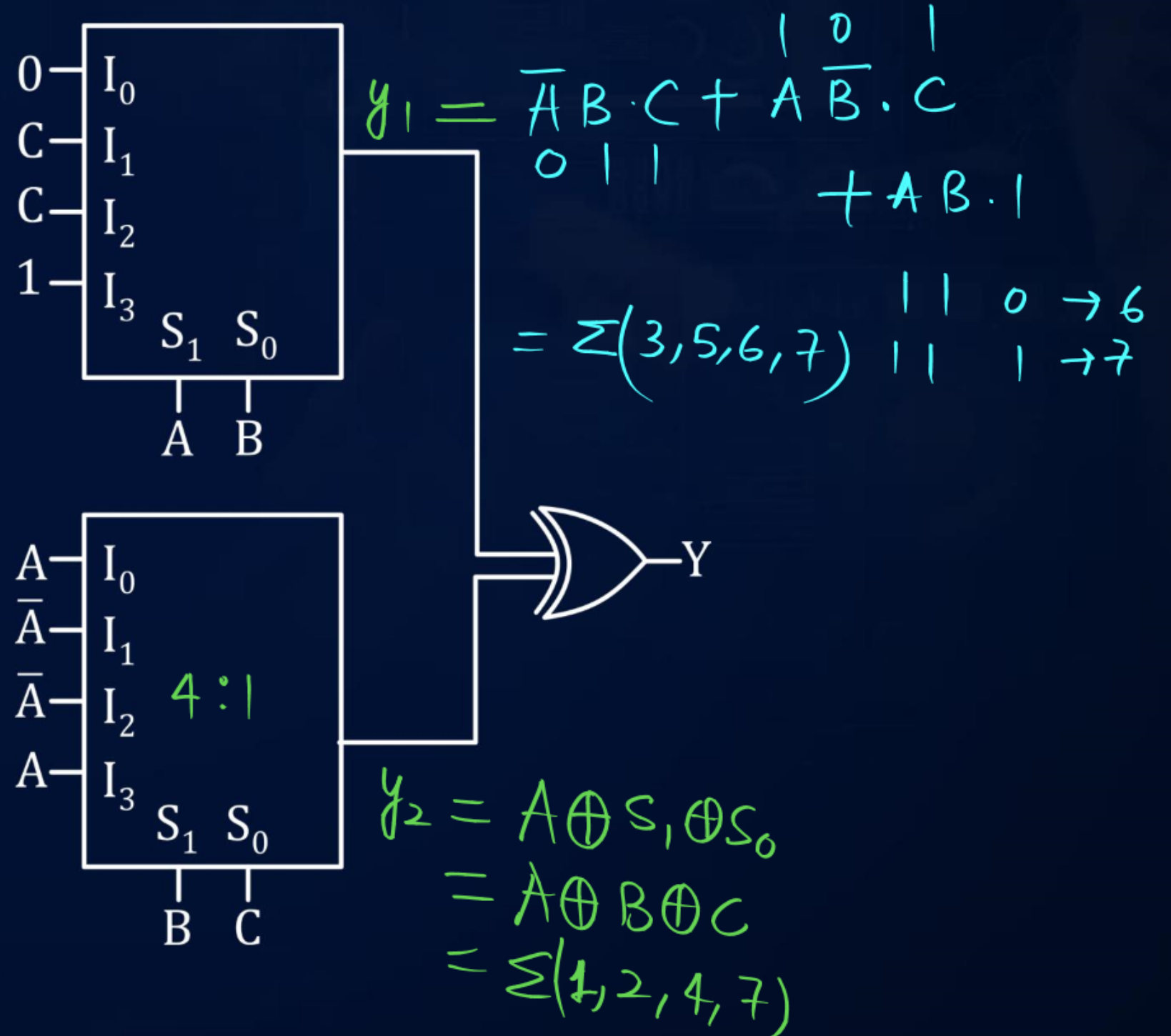
$$Y = Y_1 \oplus Y_2$$
$$= \sum(1, 2, 3, 4, 5, 6)$$



Question

MSQ.



#Q. Find the correct equation/s.

A $AB + BC + AC = AB \oplus BC \oplus AC$ ✓✓

(A, B)

B $\bar{A} \oplus \bar{B} \oplus AB = A + B \rightarrow A \oplus B \oplus AB = (A + B)$

C $\underline{AB} \odot \underline{BC} = B(A \odot C)$ ✗✗ $AB \oplus BC = B \cdot [A \oplus C]$

D $AB + BC + \bar{A}D + \bar{B}D + CD = \overline{(A + B)}D + AB + BC$ ✗
 $= \bar{A}\bar{B}D + AB + BC$

$P = AB$
 $AB + BC + D(\bar{A} + \bar{B}) + CD$
 $\Rightarrow (P + \bar{P})(P + D) + BC + CD = AB + D + BC + CD = AB + BC + D$

Question



#Q. For the 8-bit flash type ADC, the number of resistor required is $\left(\frac{2^{10}}{2^x}\right)$. The value of x is 2

$$\begin{aligned} 8 \text{ bit} &\rightarrow \text{Resistances} \rightarrow 2^8 = \frac{2^{10}}{2^x} \\ 2^x &= 2^2 \\ x &= 2 \end{aligned}$$

Question

MSQ



#Q. For the following K-map. Find the minimized Boolean function/s.

A $\bar{A}D + BC + \bar{B}\bar{C}\bar{D} + A\bar{C}\bar{D}$ ✓✓

B $\bar{A}D + BC + A\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}$ ✓✓

C $\bar{A}D + BC + \bar{B}\bar{C}\bar{D} + AB\bar{D}$ ✓✓

D $\bar{A}D + BC + \bar{B}\bar{C}\bar{D} + A\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}$ ✗

		CD			
		$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
AB	$\bar{A}\bar{B}$	1	1	1	
	$\bar{A}B$		1	1	1
	AB	1		1	1
	$A\bar{B}$	1			

Question

MSQ.



#Q. Find the correct statement/s. (A, B, C, D)

A ✓ $A\bar{B} \oplus BC = A\bar{B} + BC$ ✓✓ $A\bar{B} \oplus BC = A\bar{B} + BC$

B ✓ $A \oplus \bar{B} \oplus AB = \bar{A}\bar{B}$ ✓✓ $A \oplus \bar{B} \oplus A \cdot B = \overline{A \oplus B \oplus A \cdot B}$
 $= \overline{A+B} = \bar{A} \cdot \bar{B}$

C ✓ Boolean function, $A \oplus B \oplus \bar{A}B$, can be implement by minimum 3 NAND gate (2-i/p gate are used).

D ✓ $\bar{A}C \oplus A\bar{C} = (\bar{A} + \bar{C})(A + C)$ ✓✓ $A \oplus B \oplus \bar{A} \cdot B = \overline{\bar{A} \oplus B \oplus \bar{A}B}$
 $= \overline{\bar{A} + B}$
 $= A \cdot \bar{B} \text{ (3 NAND)}$

$\bar{A}C \oplus A\bar{C} = \bar{A}C + A\bar{C} = A \oplus C$
 $= (\bar{A} + \bar{C})(A + C)$

Question



#Q. Find the summation of PI and EPI terms in the following K-map.

A 6

B 8

C 10

D 12

PI $\rightarrow 6$
EPI $\rightarrow 2$

		YZ			
		$\bar{Y}\bar{Z}$	$\bar{Y}Z$	YZ	$Y\bar{Z}$
WX	$\bar{W}\bar{X}$	1	1		
	$\bar{W}X$		1	1	
	WX			1	1
	$W\bar{X}$				1

Question



#Q. If roots of an equation $x^2 - 10x + 26 = 0$ are 4 and 7 then base is (11).

$$x^2 - (\alpha + \beta)x + \alpha \cdot \beta = 0$$

$$(\alpha)_n + (\beta)_n = (10)_n$$


$$\begin{array}{r} (4)_{11} \\ + (7)_{11} \\ \hline (10)_{11} \end{array}$$

Question



#Q. The MOD. no. of the given Counter is 5.

down counter

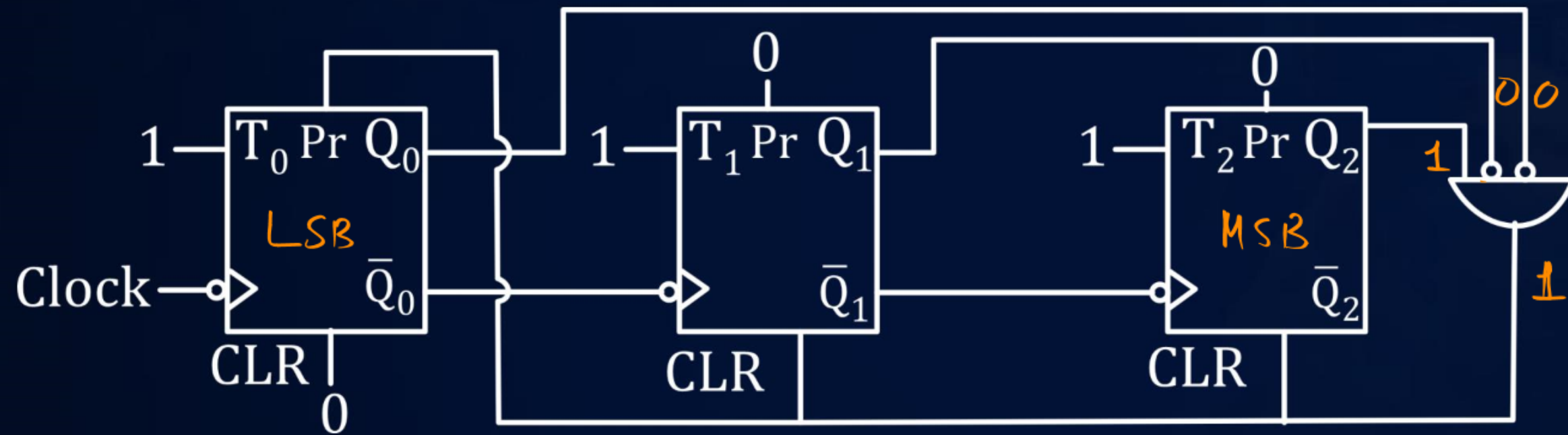

Handwritten truth table for the counter:

Q_2	Q_1	Q_0
0	0	1
0	0	0
1	1	1
1	1	0
1	0	1
1	0	0

MOD no. 5.

Question




#Q. Find the value of $f_{\max}$ for proper working.

$t_{\text{set-up}} = t_{\text{hold}} = 1 \text{ ns}$. CC stands for combinational circuit.

Circuit	Td
Flip-Flop	1ns
CC ₀	2ns
CC ₁	6 ns
CC ₂	8 ns

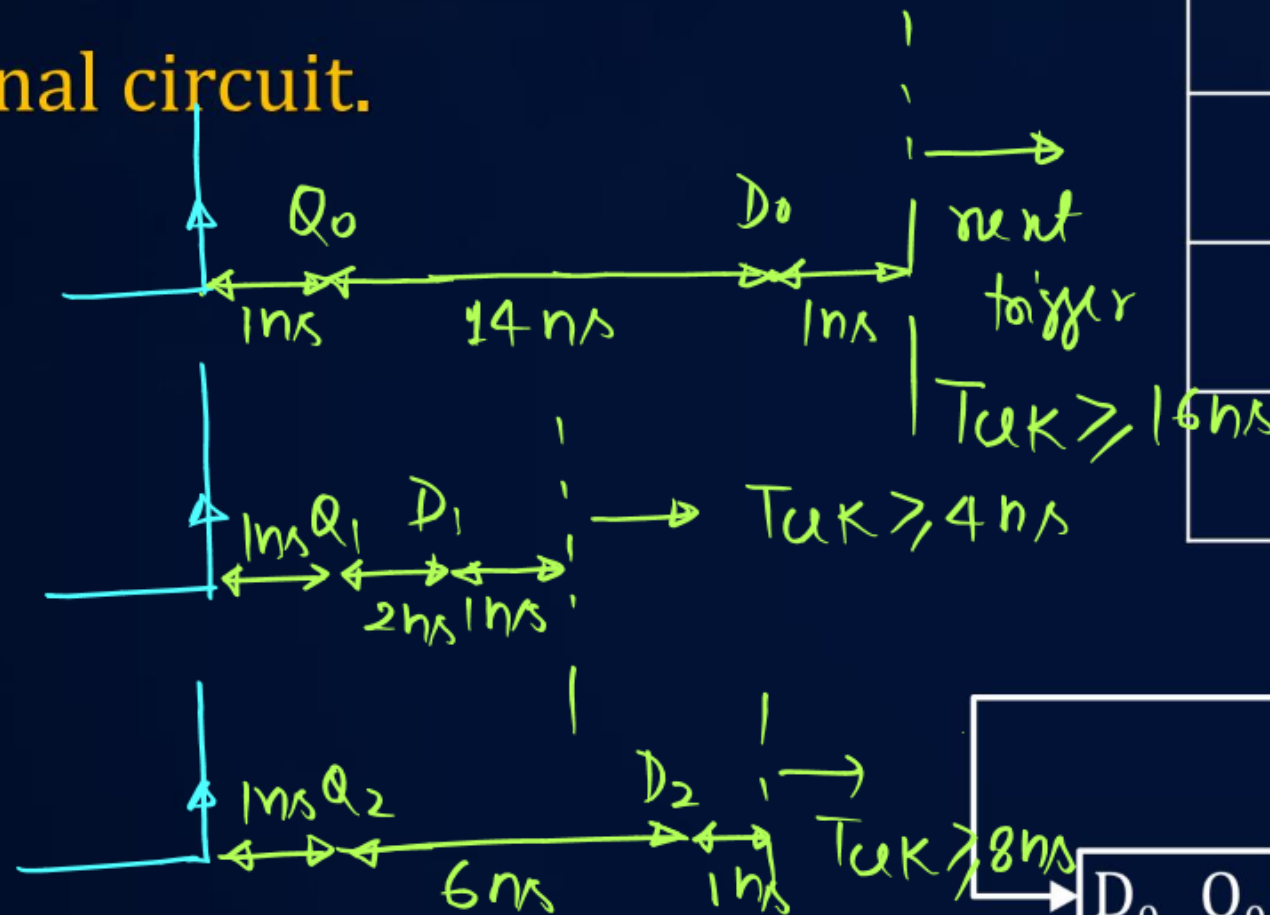
- A** 20 MHz
- B** 33.33 MHz
- C** 62.5 MHz
- D** 67.67 MHz



Overall $T_{\text{clk}} \geq 16 \text{ ns}$

$$f_{\text{clk}} \leq \frac{1}{16 \text{ ns}}$$
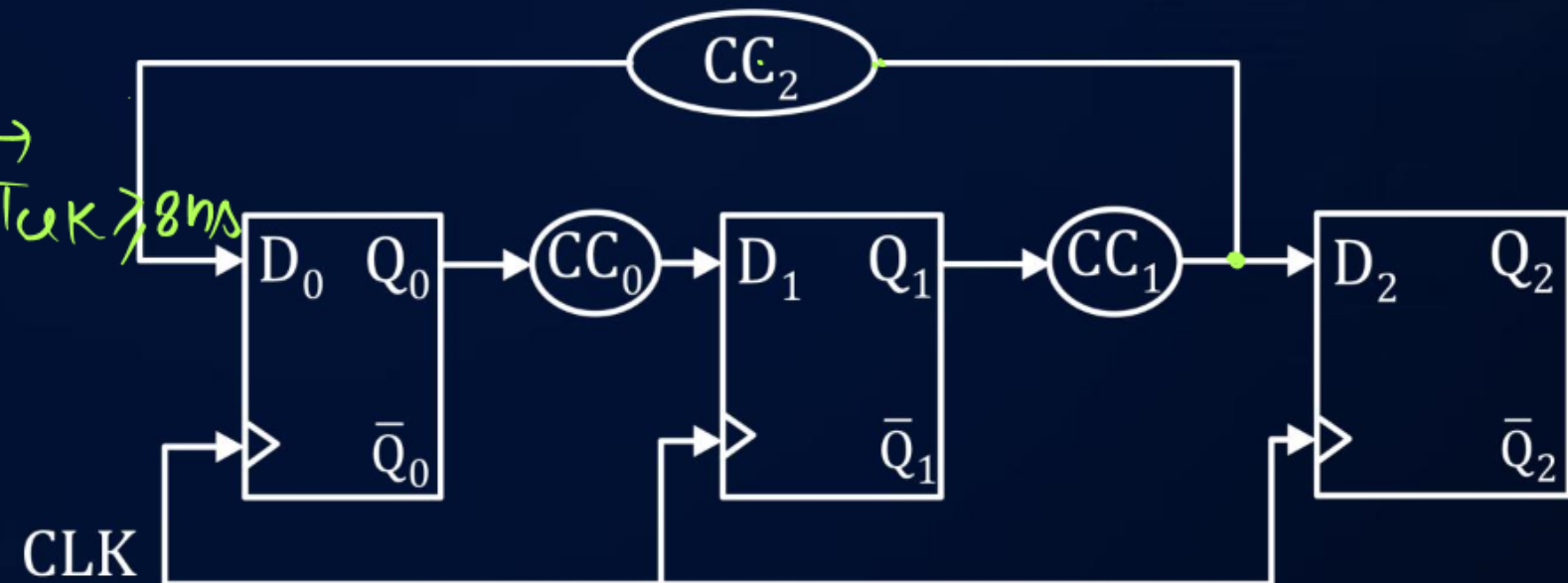
$$(f_{\text{clk}})_{\max} = \frac{1}{16 \text{ ns}} = \frac{10^3}{16} \text{ MHz}$$



Question



#Q. P, Q are the integers corresponding to the 4-bit binary number 1110 considered in 1's complement and 2's complement representations, respectively. The 5-bit 1's complement representation of (Q - P) is?

A 11111

B 11011

C 11110

D 11100

$$P = (1110)_2 \xrightarrow{1's} (0001)_2$$
$$P = (-1)_{10} \quad (+1)_{10}$$

$$00001 \xrightarrow{1's} (11110)_2$$
$$(1)_{10} \quad (-1)_{10}$$

$$Q = (1110)_2 \xrightarrow{2's} (0010)_2$$
$$(-2)_{10} \quad (+2)_{10}$$

$$Q - P = -2 - (-1)$$
$$= (-1)_{10}$$

Question



#Q. Consider the signed binary number $A = 01010110$ and $B = 11101100$ where B is the 1's complement and MSB is the sign bit, then the value of $-A - B$ in 2's complement format is

- A** 10111100 10 | 0 | 0 | 0
 + 00010011
- B** ✓ 10111101 (10111101)₂
- C** 01000010
- D** None of the above

$$A = (01010110)_2$$

↓ 2's

$$(10101010)_2 = -A$$

$$B = (11101100)_2 \xrightarrow{1's} (00010011)_2 = (-B)$$

$$-B = (00010011)_2 \xrightarrow{2's} (11101101)_2 \xleftarrow{2's} (11101101)_2$$

$B \text{ in } 2's$

$$(-A) + (-B)$$

Question



#Q. Which of the following notations have same representation of $+0$ and -0 ?

- A** 1's complement with radix of number being 2
- B** 7's complement with radix of number being 8
- C** 9's complement with radix of number being 10
- D** 10's complement with radix of number being 10

H.W

Question



#Q. The frequency at the output of the following cascaded circuit is _____ Hz

- A** 100
- B** 125
- C** 150
- D** 200




Question


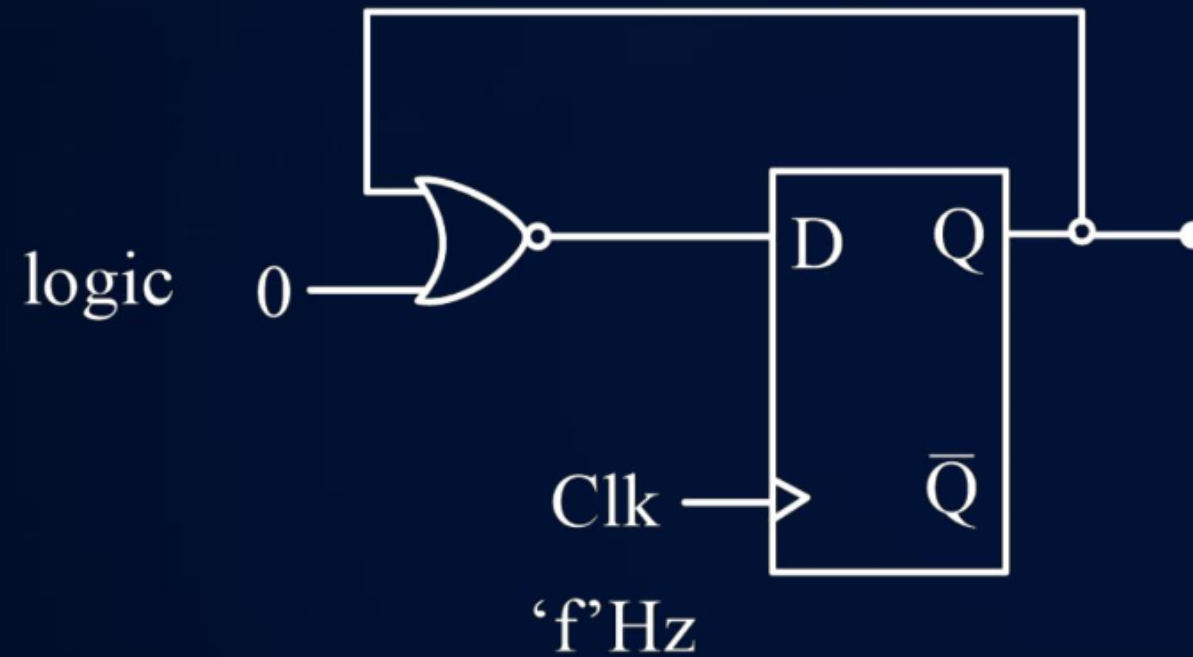
#Q. For the circuit shown below. If the clock frequency is 'f' Hz then frequency of the output Q is

- A** f
- B** $2f$
- C** $f/2$
- D** $f/3$



H.W


Question



#Q. The mod number of the given counter

Assume initially counter is let to 1011

- A** 2
- B** 4
- C** 6
- D** 8

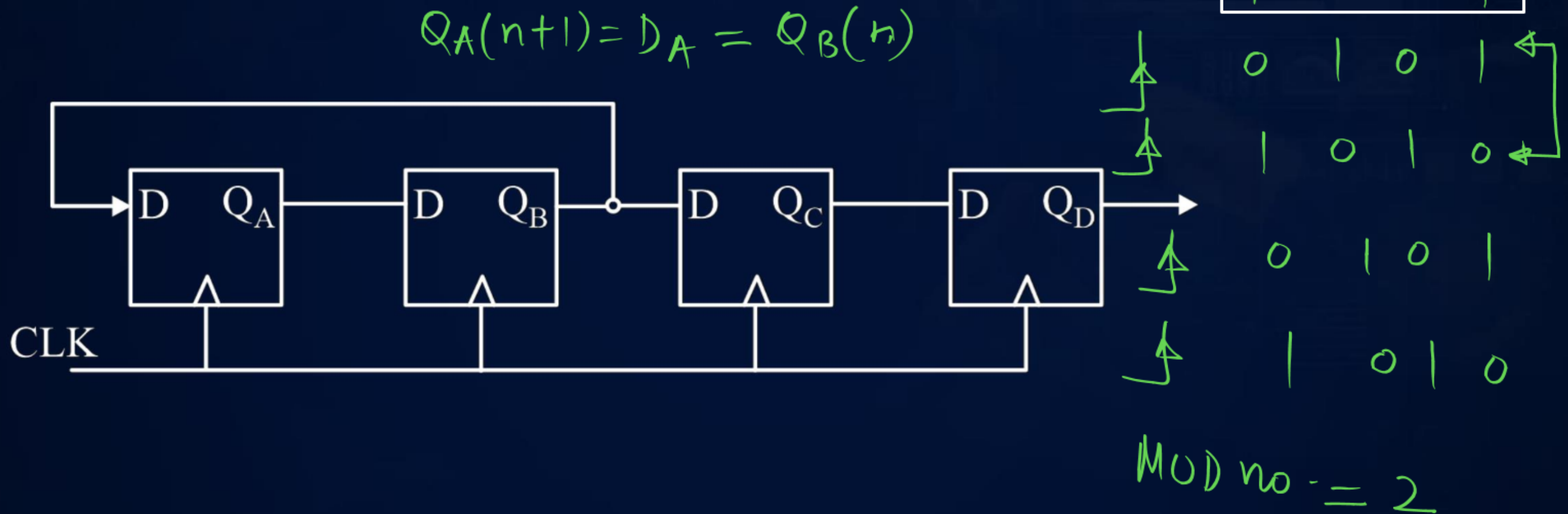


Question


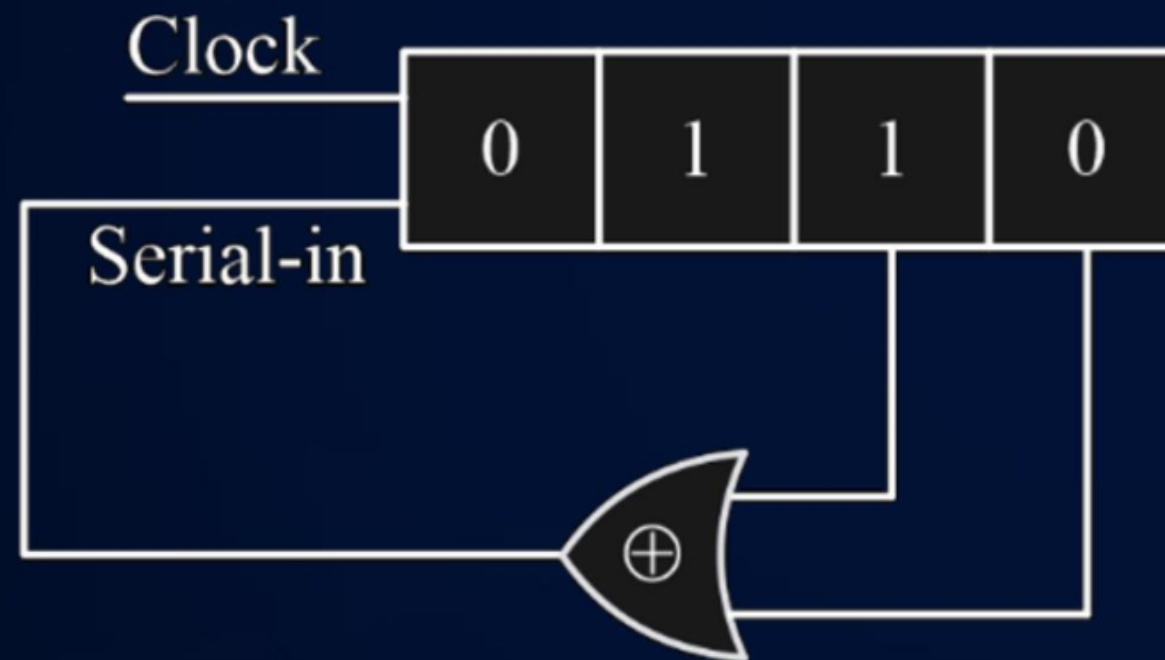
#Q. Consider the following shift right register.

The initial contents of the 4-bit serial-in parallel out, shift right register shown above are 0110. What will be the contents of the register after 3 clock pulses ?

- A** 0000
- B** 0101
- C** 1010
- D** 1111




H.W

Question



#Q. The clock frequency applied to the digital circuit shown in figure below is 50 kHz.
If initial state of the flipflop output 'Q' is '0'.
The frequency of the output wave form at 'Q' in kHz is _____

- A** 25
- B** 0
- C** 16.67
- D** 33.33

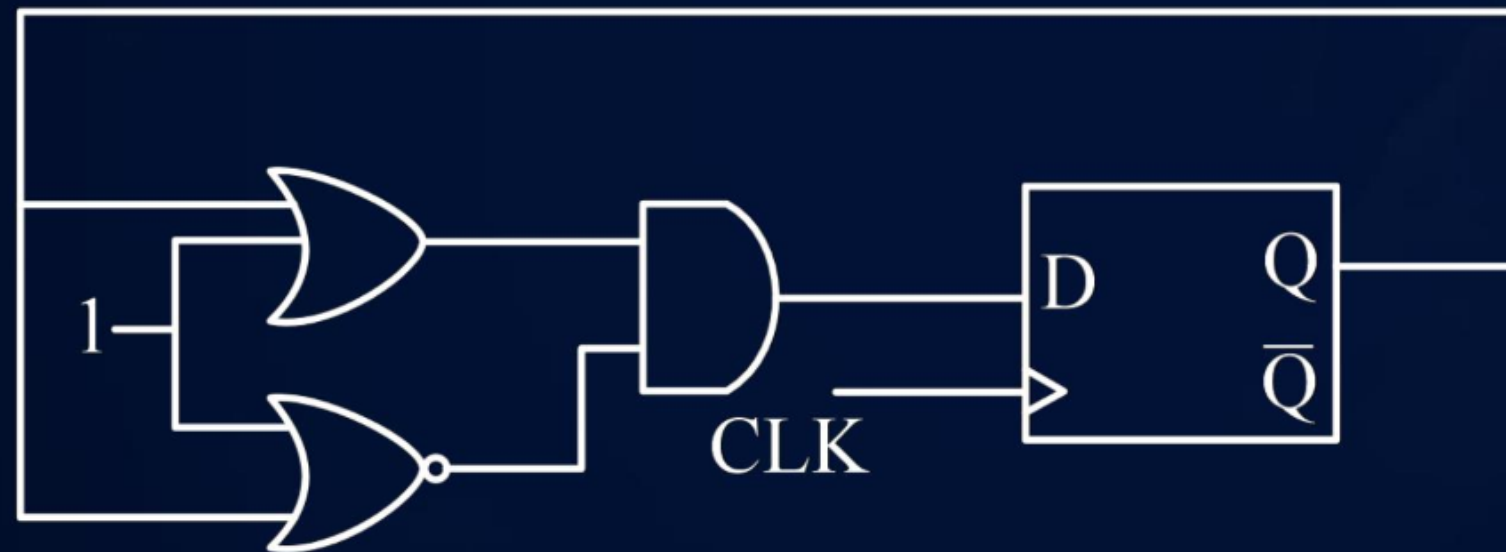

H.W


Question


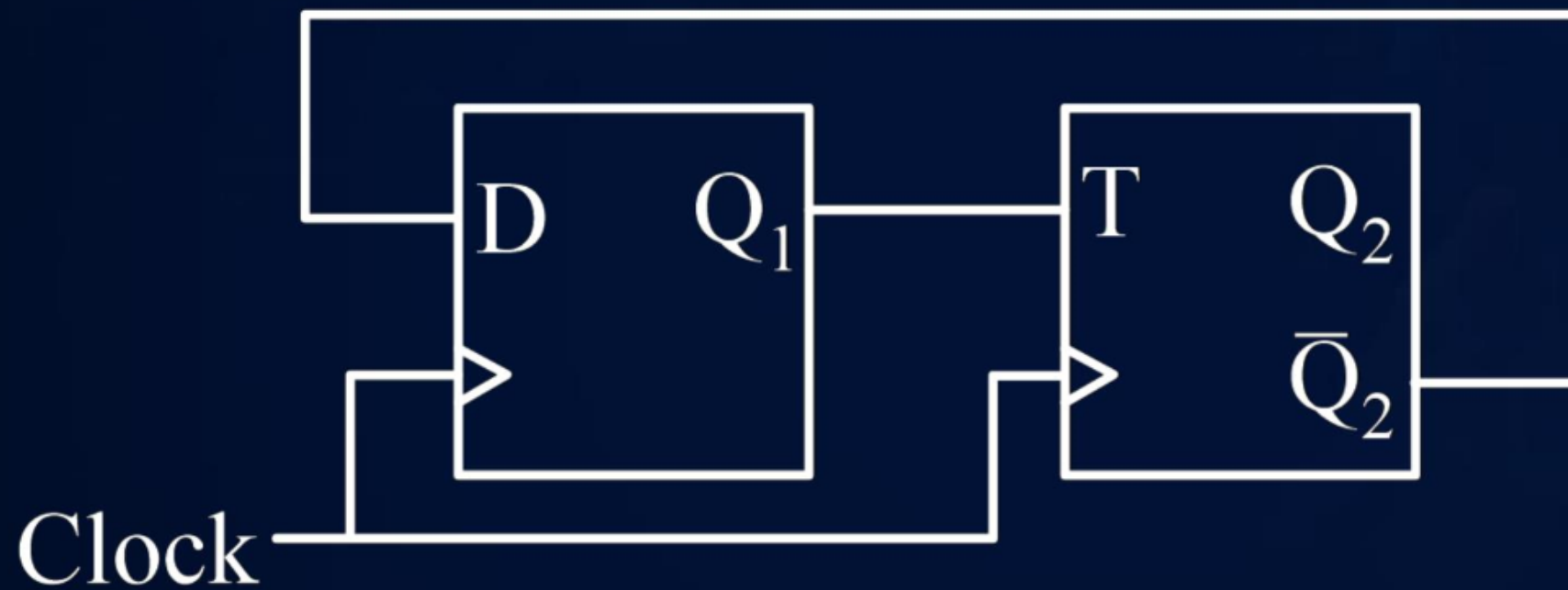
#Q. Assuming $Q_1Q_2 = 00$ initially for the following sequential circuit, then the duty cycle for wave form obtained at $\bar{Q}_2$ in % is

$$Q_1(n+1) = D_1 = \bar{Q}_2(n)$$

$$Q_2(n+1) = T_2 \oplus Q_2(n) = Q_1(n) \oplus Q_2(n)$$



	Q_1	Q_2
Initial	0	0
1st clock	1	0
2nd clock	1	1
3rd clock	0	0

$$Q_2 \rightarrow T_{off} = 2T_{clk}$$

$$T_{on} = 1T_{clk}$$

$$\bar{Q}_2 \rightarrow T_{on} = 2T_{clk}$$

$$T_{off} = 1T_{clk}$$

$$\% \text{ duty cycle} = \frac{2T_{clk}}{3T_{clk}} \times 100$$

$$= 66.67\%$$

A 66.67

B 33.33



C 50

D 25

Question


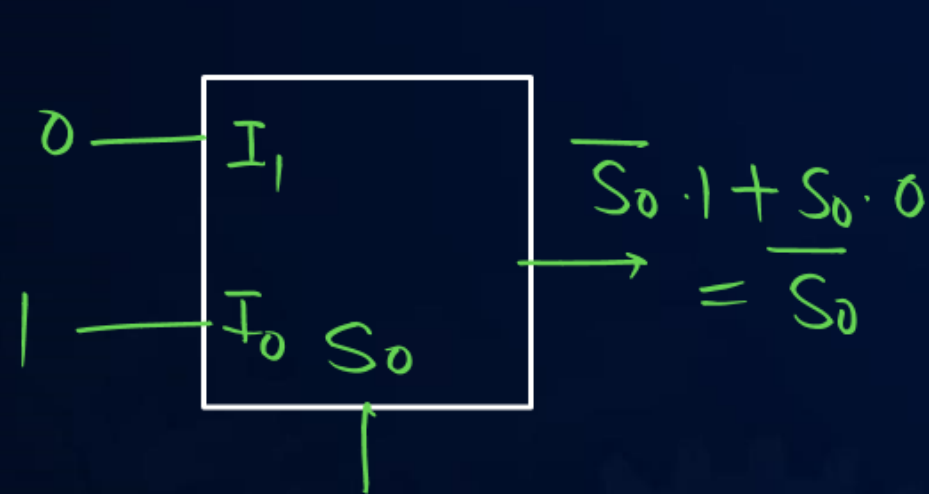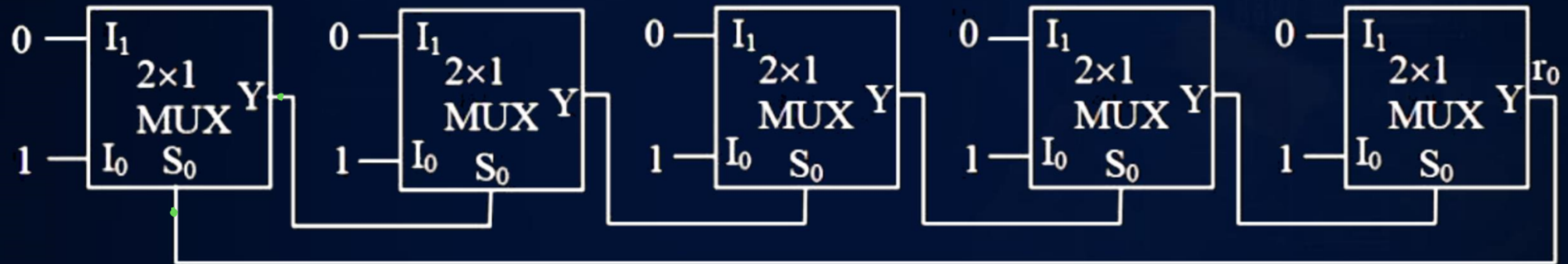
#Q. In the multiplexer-based circuit shown below, the average propagation delay of each MUX is 25 nsec. The frequency of output signal r_0 is 4 MHz.



Handwritten timing diagram showing a square wave signal A passing through five inverters to produce output r_0 . The output r_0 is the complement of A .


$$f = \frac{1}{2 \times 5 \times 25 \text{ ns}} = \frac{1}{250 \text{ ns}} = \frac{10^3}{250} \text{ MHz} = 4 \text{ MHz}$$

Question


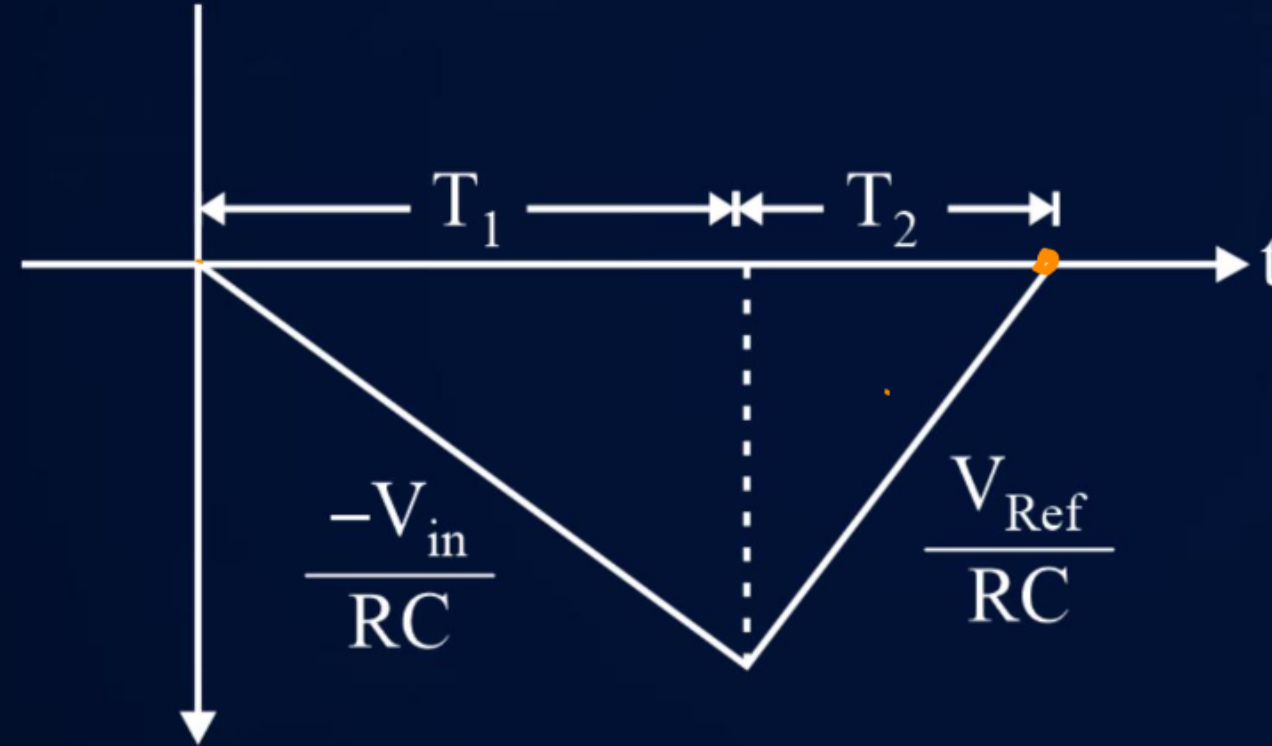
#Q. Consider integrator of dual slope integrating ADC have output as shown below:
Assume the value of input voltage (V_i) as 50 mV and reference voltage (V_R) as 100 mV. If the value of T_1 is 50 ms, then value of T_2 will be

- A** 50 ms
- B** 25 ms
- C** 70 ms
- D** 12.5 ms



$$\begin{aligned}\frac{T_2}{T_1} &= \frac{V_a}{V_{ref}} \\ T_2 &= T_1 \times \frac{V_a}{V_{ref}} \\ &= 50 \times \frac{50}{100} \\ &= 25 \text{ ms}\end{aligned}$$

Thank
You